

课程编号: 101051247 北京理工大学 2022 — 2023 学年 第 二 学期

**2022 级 电路分析基础 (全英文) 课程试卷 A**

**参考答案和评分标准**

开课学院: 集成电路与电子学院 任课教师: 邓小英

试卷用途: ☐ 期中 ☒ 期末 ☐ 补考 ☐ 重修

考试形式: ☐ 开卷 ☐ 半开卷 ☒ 闭卷

考试日期: 2023 年 5 月 23 日 所需时间: 120 分钟

考试允许带: 计算器和必要的文具 入场

班级: \_\_\_\_\_ 学号: \_\_\_\_\_ 姓名: \_\_\_\_\_

考生承诺: “**我确认本次考试是完全通过自己的努力完成的。**”

考生签名: \_\_\_\_\_

题序	1	2	3	4	5	6	7	8	9	总分
满分	10	12	12	12	10	12	12	10	10	100
得分										

注意:

1. 试题共 9 题, 共 6 页 (包含此页);
2. 所有试题答案都写在相应空白位置处, 要写清过程, 结果若为小数需保留 1 位小数。

1. (10 points) For the circuit shown in Fig.1,

(1) Find  $v_a$  and  $v_b$ ;

(2) If a  $10\Omega$  resistor is connected between  $a$  and  $b$ , find  $i_{ab}$ .

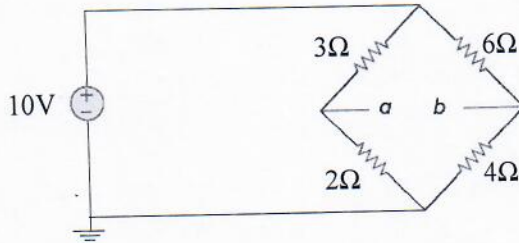


Fig.1

$$(1) \quad v_a = \frac{2}{2+3} \times 10 = 4V \quad 3\frac{1}{2}$$

$$v_b = \frac{4}{6+4} \times 10 = 4V \quad 3\frac{1}{2}$$

$$(2) \quad \because v_a = v_b, \quad R_{ab} = 10\Omega$$

$$\therefore i_{ab} = \frac{0}{10} = 0A \quad 4\frac{1}{2}$$

2. (12 points) For the circuit shown in Fig.2,

(1) find  $v_o$  by the nodal analysis;

(2) calculate the power developed by the dependent source, and determine whether the power is supplied or absorbed.

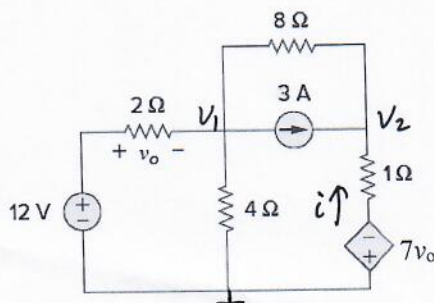


Fig.2

(1) Add the reference node as shown in Fig.2

$$\begin{cases} \frac{v_1}{4} + \frac{v_1 - 12}{2} + 3 + \frac{v_1 - v_2}{8} = 0 & 2\frac{1}{2} \\ \frac{v_2 - (-7v_o)}{1} - 3 + \frac{v_2 - v_1}{8} = 0 & 2\frac{1}{2} \\ 12 - v_1 = v_o & 2\frac{1}{2} \end{cases}$$

$$\therefore v_o = 84V, \quad v_2 = 60 - 7v_o = -528V \quad 2\frac{1}{2}$$

$$(2) \quad i = \frac{-7v_o - v_2}{1} = -7 \times 84 - (-528) = -60A \quad 1\frac{1}{2}$$

$$P = 7v_o \cdot i = -35280W \quad 2\frac{1}{2}$$

supply power  $1\frac{1}{2}$



3. (12 points) In the steady-state circuit shown in Fig.3,  $v_s(t) = 12 \cos \omega t$  V.

- (1) Find and draw the Norton equivalent of the left-part circuit from terminals  $ab$ ;
- (2) Find the resonant frequency  $\omega_0$ , the quality factor  $Q$  and bandwidth  $B$  as seen by the inductor;
- (3) Find the cut-off frequencies  $\omega_1$ ,  $\omega_2$  and the average power dissipated at  $\omega_0$ ,  $\omega_1$ ,  $\omega_2$ .

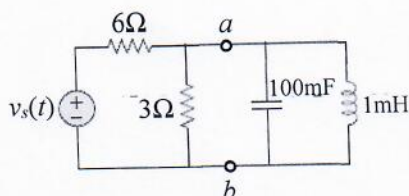



Fig. 3

(1) As seen from terminals  $ab$

$$R_0 = 3 \parallel 6 = 2 \Omega \quad 2 \text{分}$$

$$i_{sc} = \frac{v_s(t)}{6} = 2 \cos \omega t \text{ A} \quad 2 \text{分}$$

Norton equivalent:

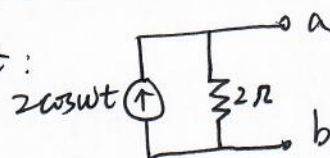

$$(2) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{10^3}{10} = 100 \text{ rad/s} \quad 1 \text{分}$$

$$B = \frac{G}{C} = \frac{1}{R_0 C} = \frac{10}{2} = 5 \text{ rad/s} \quad 1 \text{分}$$

$$Q = \frac{\omega_0}{B} = \frac{100}{5} = 20 \quad 1 \text{分}$$

$$(3) \omega_1 = 100 - \frac{5}{2} = 97.5 \text{ rad/s} \quad 1 \text{分}$$

$$\omega_2 = 100 + \frac{5}{2} = 102.5 \text{ rad/s} \quad 1 \text{分}$$

$$P_{\omega_0} = I_{rms}^2 R_0 = \left(\frac{2}{\sqrt{2}}\right)^2 \cdot 2 = 4 \text{ W} \quad 1 \text{分}$$

$$P_{\omega_1} = P_{\omega_2} = \frac{1}{2} P_{\omega_0} = 2 \text{ W} \quad 1 \text{分}$$

4. (12 points) The switch in Fig.4 has been open for a long time, and is open at  $t=0$ .

- (1) Determine  $i(0^+)$ ,  $v(0^+)$ ,  $\frac{di(0^+)}{dt}$  and  $\frac{dv(0^+)}{dt}$ ;

- (2) For  $t > 0$ , write the second-order circuit equation about  $v(t)$  and determine what type of damping this circuit exhibits (over-damped/under-damped/critically-damped).

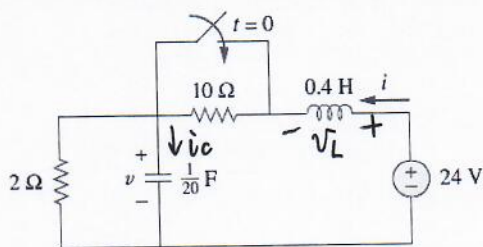


Fig. 4

$$(2) \begin{cases} \frac{v}{2} + \frac{1}{20} \frac{dv}{dt} = i & \text{①} \\ 0.4 \frac{di}{dt} = 24 - v & \text{②} \end{cases} \quad 1 \text{分}$$

Take the derivative of ①:

$$\frac{1}{2} \frac{dv}{dt} + \frac{1}{20} \frac{d^2v}{dt^2} = \frac{di}{dt} \quad \text{③} \quad 2 \text{分}$$

$$\text{Substitute ③ into ②: } \frac{dv}{dt^2} + 10 \frac{dv}{dt} + 50v = 1200$$

$$\therefore \text{characteristic equation } s^2 + 10s + 50 = 0$$

$$\Delta = 10^2 - 4 \times 50 = -100 < 0 \quad 1 \text{分}$$

$\therefore$  under-damped case.  $1 \text{分}$

$$(1) i(0^+) = i(0^-) = \frac{24}{12} = 2 \text{ A} \quad 1 \text{分}$$

$$v(0^+) = v(0^-) = 2 \text{ A} \times 2 \Omega = 4 \text{ V} \quad 1 \text{分}$$

$$v_L(0^+) = 24 - v(0^+) = 20 \text{ V}$$

$$\therefore \frac{di}{dt} \bigg|_{t=0^+} = \frac{v_L(0^+)}{L} = 50 \text{ A/s} \quad 2 \text{分}$$

$$i_c(0^+) = i - \frac{v(0^+)}{2} = 2 - \frac{4}{2} = 0$$

$$\therefore \frac{dv}{dt} \bigg|_{t=0^+} = \frac{i_c(0^+)}{C} = 0 \quad 2 \text{分}$$

5. (10 points) For the circuit in Fig.5, what resistor connected across terminals a-b will absorb maximum power from the circuit? What is the maximum power?

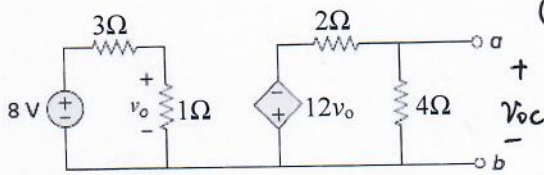


Fig.5

(1) Find the Thevenin equivalent from ab:

$$v_o = \frac{1}{1+3} \times 8 = 2V$$

$$v_{oc} = -12v_o \times \frac{4}{2+4} = -24 \times \frac{2}{3} = -16V$$

$$i_{sc} = -\frac{24}{2} = -12A$$

$$R_o = \frac{-16}{-12} = \frac{4}{3}\Omega$$

$$\text{or } R_o = 2 \parallel 4 = \frac{4}{3}\Omega$$

(2) When  $R_L = \frac{4}{3}\Omega$ , 2分

$$P_{max} = \frac{V_{oc}^2}{4R_o} = \frac{16^2}{4 \times \frac{4}{3}} = 48W$$

6. (12 points) In the steady-state circuit shown in Fig.6,  $u_s(t) = 2\cos(1000t + 30^\circ)$ . Calculate the steady-state response  $i(t)$ .

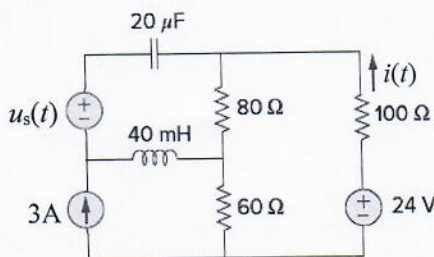


Fig.6

(1) 24V acting alone:

$$i_1(t) = \frac{24}{100 + 80 + 60} = \frac{24}{240} = 0.1A$$

(2) 3A acting alone:




$$i_2(t) = -3 \times \frac{60}{60 + 180} = -\frac{3}{4}A$$

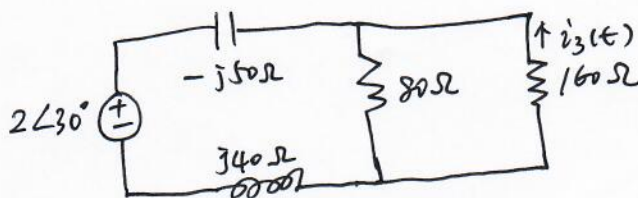(3)  $u_s(t) = 2\cos(1000t + 30^\circ)$  acting alone:

$$j\omega L = j1000 \times 40 \times 10^{-3} = j40\Omega$$

$$-j\frac{1}{\omega C} = -j\frac{1}{1000 \times 20 \times 10^{-6}} = -j50\Omega$$



$$i_3 = \frac{80}{160 + 80} \times \frac{-2\angle 30^\circ}{j40 - j50 + 80 \parallel 160}$$

$$= \frac{1}{3} \times \frac{2\angle -150^\circ}{\frac{160}{3} - j10}$$

$$= \frac{2\angle -150^\circ}{160 - j30} = \frac{2\angle -150^\circ}{162.8\angle 10.6^\circ}$$

$$= 0.012\angle -139.4^\circ A$$

$$\therefore i_3(t) = 0.012\cos(1000t - 139.4^\circ) A$$

4/6

$$\therefore i(t) = -0.65 + 0.012\cos(1000t - 139.4^\circ) A$$

2分



7. (12 points) Refer to the circuit shown in Fig.7,

- (1) What is the power factor of the load Z? Is it a lagging or leading pf?
- (2) What are the average power and the reactive power developed by the load Z?
- (3) What element should be connected with the load Z that will raise the power factor to 0.95? Calculate the value of the capacitance (if the element is a capacitor) or the inductance (if the element is an inductor).



Fig. 7

$$(1) \text{ pf} = \cos \theta = \frac{3}{\sqrt{3^2 + 4^2}} = \frac{3}{5} \quad \text{lagging pf, inductive load}$$

$$(2) P = \left| \frac{120}{5} \right|^2 \times 3 = 24^2 \times 3 = 1728 \text{ W}$$

$$Q = \left| \frac{120}{5} \right|^2 \times 4 = 2304 \text{ VAR}$$

(3) Capacitor

$$Q_2 = P \cdot \tan \theta_2 = 1728 \times \frac{\sqrt{1 - 0.95^2}}{0.95} = 563.9 \text{ VAR}$$

$$Q_c = 563.9 - 2304 = -1740.1 = -\omega C V^2 = -2\pi \times 60 \times C \times 120 \times 120$$

$$C = \frac{-1740.1}{-120 \times 2\pi \times 60 \times 120} = 0.32 \text{ mF} = 321 \text{ }\mu\text{F}$$

8. (10 points) Simplify the following two-terminal networks in Fig. 8.


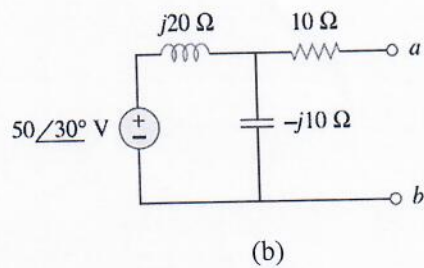
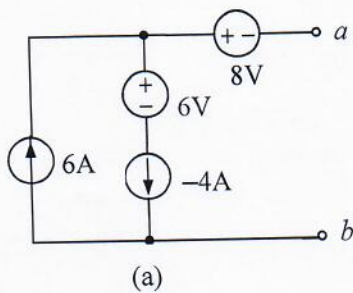



Fig. 8

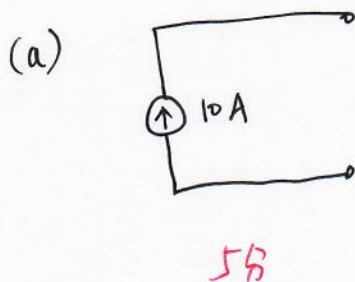

$$(b) \quad V_{oc} = 50\angle 30^\circ \times \frac{-j10}{j20 - j10} = 50\angle -150^\circ \text{ V} \quad 2\frac{1}{2}\text{分}$$

$$Z_o = 10 + j20 \parallel (-j10) \quad 2\frac{1}{2}\text{分}$$
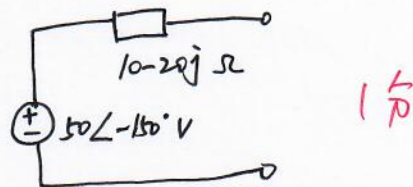
$$= 10 + \frac{20 \times 10}{j10} = 10 - 20j$$



9. (10 points) In the circuit shown in Fig. 9, the switch has been open for a long time, and is closed at  $t=0$ , find the capacitor voltage  $v(t)$  for  $t > 0$ .

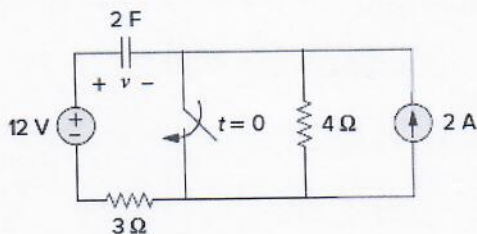


Fig. 9

$$t < 0, \quad V(0_-) = 12 - 4 \times 2 = 4 \text{ V} = V(0_+) \quad 2\frac{1}{2}\text{分}$$

$$t \rightarrow \infty, \quad v(\infty) = 12 \text{ V} \quad 2\frac{1}{2}\text{分}$$

$$R_o = 3 \Omega \Rightarrow \tau = R_o C = 6 \text{ s} \quad 2\frac{1}{2}\text{分}$$

$$v(t) = v(\infty) + [v(0_+) - v(\infty)] e^{-\frac{t}{\tau}} \quad 2\frac{1}{2}\text{分}$$

$$= 12 - 8e^{-\frac{t}{6}} \text{ V}, t > 0 \quad 2\frac{1}{2}\text{分}$$