

## 2021 级 电路分析基础（全英文） 课程试卷 B

开课学院: 集成电路与电子学院 任课教师: 邓小英

试卷用途: ☐ 期中 ☒ 期末 ☐ 补考 ☐ 重修

考试形式: ☐ 开卷 ☐ 半开卷 ☒ 闭卷

考试日期: 2022 年 5 月 29 日 所需时间: 120 分钟

考试允许带: 计算器和必要的文具 入场

班级: 学号: 姓名:

### 在线考试诚信承诺书

考试是对知识与能力的检验,也是对道德素质的检验。在线考试也必须恪守诚信原则。

我已成功下载本次《电路分析基础(全英文)》课程期末考试试卷,并承诺在考试过程中严于律己,自觉遵守以上考试规则,诚信考试。

承诺人(签字):

年 月 日

题序	1	2	3	4	5	6	7	8	9	总分
满分	8	8	7	8	7	8	8	8	8	70
得分										

注意:

1. 试题共 9 题, 共 4 页 (包含此页);
2. 所有试题都要写清过程 (用英文), 结果保留 1 位小数即可。

1. (8 points) For the circuit shown in Fig.1, (1) find  $V_o$  ; (2) calculate the power developed by the dependent source, and determine whether the power is supplied or absorbed.

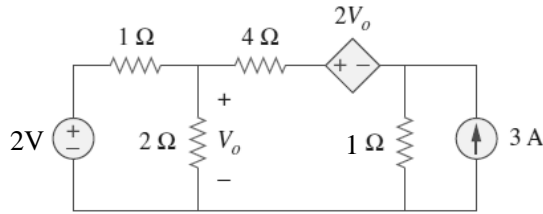


Fig.1

2. (8 points) In the steady-state circuit shown in Fig.2,  $R=4\Omega$ ,  $L=1\text{H}$ ,  $v_s(t) = \cos \omega t$  V .  
 (1) Determine the value of  $C$  that will cause the resonance at  $\omega_0=100\text{rad/s}$  for the circuit ;  
 (2) Calculate the quality factor  $Q$  at resonance and the half-power frequencies  $\omega_1$ ,  $\omega_2$  ;  
 (3) Find the transfer function  $\mathbf{H}(\omega) = \dot{\mathbf{V}}_o / \dot{\mathbf{V}}_s$ , draw the sketch plot of  $|\mathbf{H}(\omega)|$  and determine the type of filter (lowpass/highpass/bandpass/bandstop).

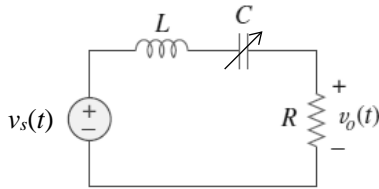


Fig. 2

3. (7 points) The switch in Fig.3 has been open for a long time, and is closed at  $t=0$ .

- (1) Determine  $v(0^+)$  and  $i(0^+)$ ,  $\frac{dv(0^+)}{dt}$  and  $\frac{di(0^+)}{dt}$  ;  
 (2) For  $t > 0$ , write the second-order circuit equation about  $v(t)$  and determine what type of damping this circuit exhibits (over-damped/under-damped/critically-damped).

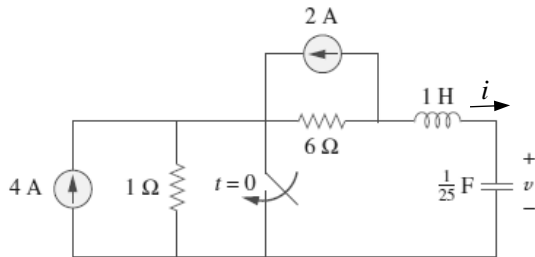


Fig.3

4. (8 points) Find the value of  $R$  that enables the circuit shown in Fig.4 to deliver the maximum power to terminals a-b. Then calculate the power delivered to  $R$ .

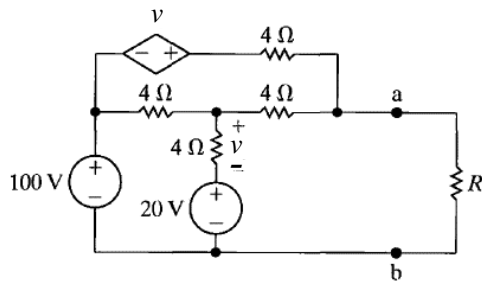


Fig.4

5. (7 points) Calculate the current  $I_0$  when  $R=28\text{k}\Omega$  and  $R=100\text{k}\Omega$ , respectively.

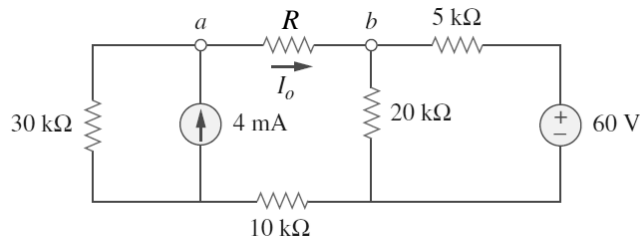


Fig.5

6. (8 points) For the steady-state circuit shown in Fig.6, find  $i_o(t)$ .

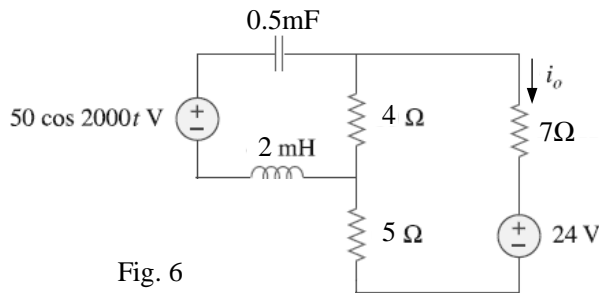


Fig. 6

7. (8 points) The sinusoidal circuit is shown in Fig. 7.

- (1) Find the total average power  $P$  developed by load 1 and load 2.
- (2) Find the total reactive power  $Q$  developed by load 1 and load 2.
- (3) Calculate the power factor of the parallel combination.
- (4) What element should be connected with the load 1 and load 2 that will raise the power factor to 1? Calculate the value of the capacitance (if the element is a capacitor) or the inductance (if the element is an inductor).



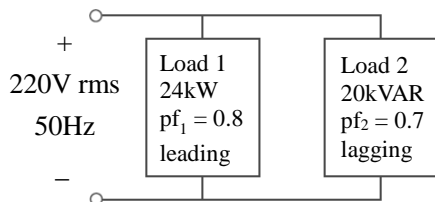


Fig. 7

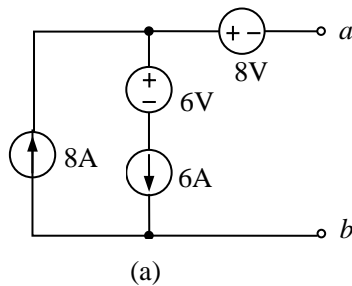8. (8 points) Simplify the following circuits in Fig.8.



(a)

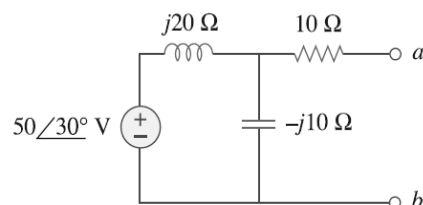

(b)

Fig.8

9. (8 points) In the circuit shown in Fig.9,  $U_s = 10\text{V}$ ,  $R_1 = 6\Omega$ ,  $R_2 = R_3 = 4\Omega$ ,  $L = 1\text{H}$ ,  $C = 2\text{F}$ , the switch has been open for a long time, and is closed at  $t = 0$ . Find the current  $i(t)$  for  $t > 0$ .

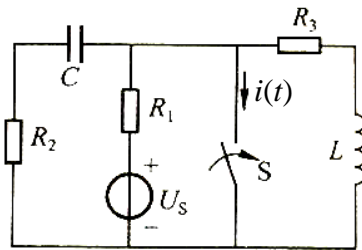


Fig.9