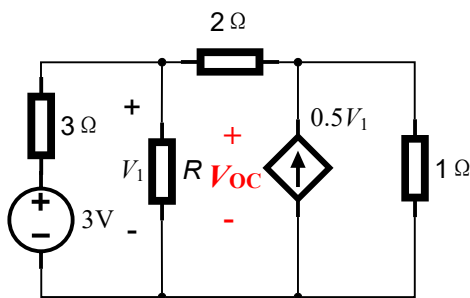


1. (4 points) In the circuit below, how much resistance of R will draw the maximum power from the circuit? Calculate the maximum power.






Open the R , transform the $0.5V_1(\text{A})$ in parallel with 1Ω into a $0.5V_1(\text{V})$ in series with 1Ω , then transform into a $0.5V_1/3(\text{A})$ in parallel with 3Ω

$$\left(\frac{1}{3} + \frac{1}{3}\right)V_{oc} = \frac{3}{3} + \frac{0.5V_{oc}}{3} \Rightarrow V_{oc} = 2\text{V}$$

$$I_{sc} = \frac{3}{3} = 1\text{A} \Rightarrow R_0 = \frac{V_{oc}}{I_{sc}} = 2\Omega$$


$$\text{When } R = R_0 = 2\Omega, P_{\max} = \frac{V_{oc}^2}{4R_0} = 0.5\text{W}$$

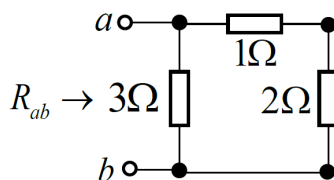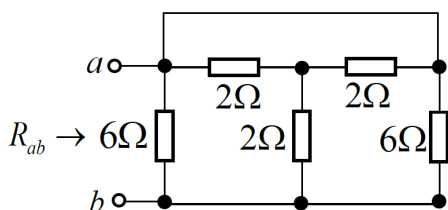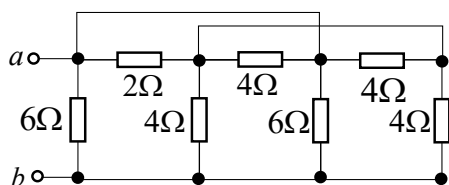2. (3 points) Find the equivalent resistance R_{ab} as seen from terminals $a-b$.



$$R_{ab} = \frac{(1+2) \times 3}{(1+2)+3} = \frac{3}{2}\Omega$$

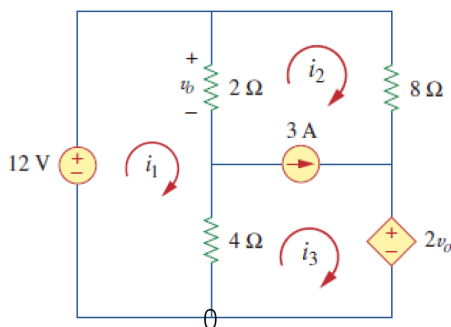3. (3 points) Calculate the power developed by the dependent source, and determine whether the power is supplied or absorbed.



$$\begin{cases} 12 = 2(i_1 - i_2) + 4(i_1 - i_3) \\ 2(i_2 - i_1) + 8i_2 + 2v_0 + 4(i_3 - i_1) = 0 \\ v_0 = 2(i_1 - i_2) \\ 3 = i_3 - i_2 \end{cases} \Rightarrow \begin{cases} i_3 = 2.5\text{A} \\ v_0 = 8\text{V} \end{cases}$$

$$P = 2v_0 \times i_3 = 40\text{W absorbed power}$$