

2. Solution:

equation of clock: $CP_0 = CP_0, CP_1 = \bar{Q}_0, CP_2 = \bar{Q}_1, CP_3 = \bar{Q}_0$

equation of state: $FF_0 = \bar{Q}_0^{n+1}, J_0 = K_0 = 1, CP_0 \downarrow$

$FF_1: J_1 = \bar{Q}_2 \bar{Q}_3, J, K_1 = 1, \bar{Q}_0 \downarrow, Q_0 \uparrow$

$FF_2: J_2 = K_2 = 1, \bar{Q}_1 \downarrow, Q_1 \uparrow$

$FF_3: J_3 = \bar{Q}_1 \bar{Q}_2, K_3 = 1, \bar{Q}_0 \downarrow, Q_0 \uparrow$

equation of state: $FF_0: Q_0^{n+1} = \bar{Q}_0^n, CP_0 \downarrow$

$FF_1: Q_1^{n+1} = (Q_2 + Q_3) \bar{Q}_1^n, Q_0 \uparrow$


$FF_2: Q_2^{n+1} = \bar{Q}_2^n, Q_1 \uparrow$

$FF_3: Q_3^{n+1} = \bar{Q}_1 \bar{Q}_2 \bar{Q}_3, Q_0 \uparrow$

equation of output: $CO = \bar{Q}_3 \bar{Q}_2 \bar{Q}_1 \bar{Q}_0 = 1Q_0 + Q_1 + Q_2 + Q_3$

Transformation table

Q_3^n	Q_2^n	Q_1^n	Q_0^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
0	0	1	1	0	1	1	0
0	1	0	0	0	0	1	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	1
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1
1	0	1	0	1	0	1	0
1	0	1	1	1	0	1	1
1	1	0	0	1	1	0	0
1	1	0	1	1	1	0	1
1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1

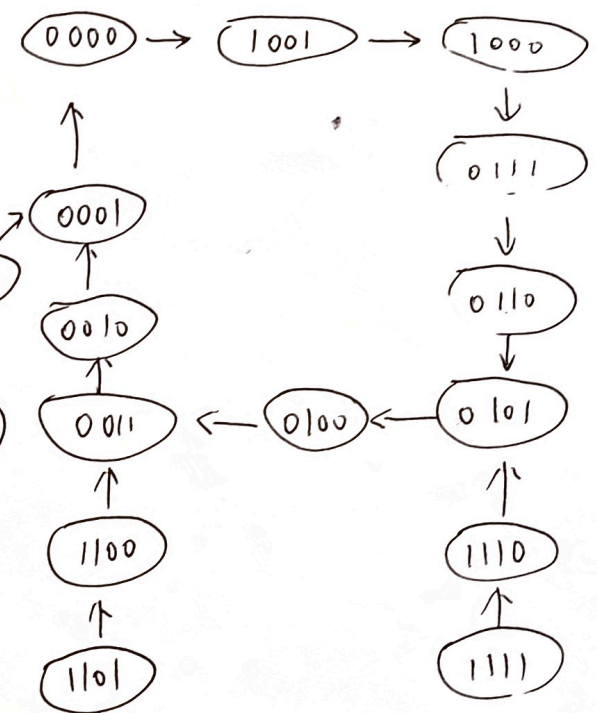

Function:
Asynchronous, Decimal subtract
Counter. Self-starting

3. solution:

clock: $CP = CP$

~~reset~~: $D_3 D_2 D_1 D_0 = 0000$

$\overline{CR} = \overline{Q_1 Q_3}$, $CO = Q_3$

$M = 1010 = 10$

Use the Asynchronous - clear method , Decimal counter.

4. solution:

The 74161(I), 74161(II) construct a 16x16 - ary counter.

clock: $CP = CP$

preset: 0

$\overline{LD} = \overline{Q_{2II} Q_{0II} Q_{1I}}$, $CO = \overline{LD}$

~~$M = 1111111111111111$~~

~~$M = 1111$~~

$M-1 = 5 \times 16 + 2 \times 16^0$

$M = 83$

use the synchronous ~~method~~ preset method. 83- ary counter.

Ch07 Assignments Digital Logic

1120230272 三天

1. Analysis the function of the sequential logic circuit.

Solution: equation of clocks: $CP_1 = CP$, $CP_2 = CP$, $CP_3 = CP$ synchronous.

equation of driver: FF₁: $J_1 = \bar{Q}_3$ $K_1 = \bar{Q}_3$

FF₂: $J_2 = Q_1$ $K_2 = Q_1$

FF₃: $J_3 = Q_1 Q_2$ $K_3 = Q_3$

equation of output: $CO = Q_3$

equation of state: $Q^{n+1} = J\bar{Q}^n + \bar{K}Q^n$


$$FF_1: Q_1^{n+1} = \bar{Q}_3 \bar{Q}_1^n + Q_3 Q_1^n = Q_3^n \odot Q_1^n$$

$$Q_2^{n+1} = Q_1^n \bar{Q}_2^n + \bar{Q}_1 Q_2^n = Q_2^n \oplus Q_1^n$$

$$Q_3^{n+1} = \bar{Q}_1 Q_2^n \bar{Q}_3^n + \bar{Q}_3 Q_3^n = \bar{Q}_1^n \bar{Q}_2^n \bar{Q}_3^n + Q_3^n$$

state transformation table.

Q_3^n	Q_2^n	Q_1^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	1	0	0	1	0
1	1	1	0	0	1

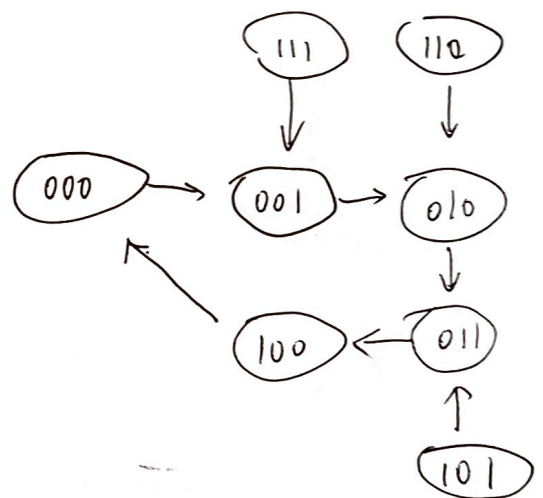

Function:

Synchronous, 5-ary additional counter

self-starting